

Physics 200

Chapter 28 DC Circuits (Homework)

1. Resistor, R_1 , is in series with resistors, R_2 and R_3 , which are in parallel. Calculate the equivalent resistance of the circuit.
2. Calculate the current through resistor, R , of the circuit in Figure P28.27 (9th edition).
3. Calculate the power of resistor, $2R$, of the circuit in Figure P28.27 (9th edition).
4. A capacitor, C , is connected in series to a resistor, R , and a battery, V . At what rate is energy being dissipated by the resistor “ t ” seconds after the battery is connected to the resistor and capacitor?
5. In Figure P28.65 (9th edition) assume the switch has closed at time, $t = 0$. If the capacitors are initially uncharged, what is the charge on capacitor, C_1 , as a function of time after the switch is closed?
6. In Figure P28.41 (9th edition) assume the switch has open for a very long time. The switch is then closed. Calculate the current through resistor, R_2 , as a function of time.
7. In Figure P28.41 (9th edition) assume the switch has closed for a very long time. The switch is then opened. Calculate the current through resistor, R_1 , as a function of time.
8. Show that, when a charged capacitor is discharged through a resistor, the total energy initially stored in the capacitor is equal to the total energy dissipated by the resistor. (Hint: integrate the power over all time for the resistor and remember that current varies with time.)