Physics 200

Chapter 32 Inductance (Homework)

- 1. Calculate the inductance per unit length of a coaxial cable. The inner conductor has a radius, a, and the outer conductor has radius, b.
- 2. A solenoid has "N" turns, has length, D, and radius, a. At what rate is the current through the solenoid changing if the inductor voltage is " V_1 "?
- 3. A toroid consists of "N" turns and has a rectangular cross section. The inner radius is "a", the outer radius is "b" and the height is "h". Calculate the inductance of the toroid.
- 4. A resistor, R, and an inductor, L, have been connected to a battery, V, for a very long time. What is the power at the resistor as a function of time after the battery has been removed?
- 5. A resistor, R, and an inductor, L, are connected to a battery, V. What is the power at the resistor as a function of time after the battery has been connected?
- 6. A resistor, R, and an inductor, L, are connected to a battery, V. After they are connected together, what is the voltage across the resistor as a function of time?
- 7. An LC circuit consists of an inductor, L, and a capacitor, C. If the maximum current is "I max", what is the maximum voltage across the capacitor?
- 8. A long thin solenoid has length, D, "N" turns per meter and carries a current, I. Determine the energy density of the solenoid's magnetic field.
- 9. Calculate the energy stored in the inductor of a charging RL circuit as a function of time after the battery, ε, has been connected.
- 10. Determine the energy stored in an infinitely long solenoid's magnetic field. The solenoid has length, D, current, I, radius, a, and "n" turns per unit length.